

Electronics & Signal Processing for Experimental Rigs

Day 2: Noise and OpAmp Circuits

Ofer Mazor, Pavel Gorelik, Navid Mousavi

HMS Research Instrumentation Core


PiN Grad Student

Lecture 2 Outline

- Questions from Lecture 1 / Assignment 1
 - *Capacitive coupling: will be addressed in this lecture*
- Noise: Sources & Solutions
 - Mechanisms behind common sources of rig noise
 - Methods for reducing each kind of noise
- Amplifiers
 - OpAmps
 - Voltage follower (buffer)
 - Gain amplifiers

Maximizing Signal Quality

Last lecture:

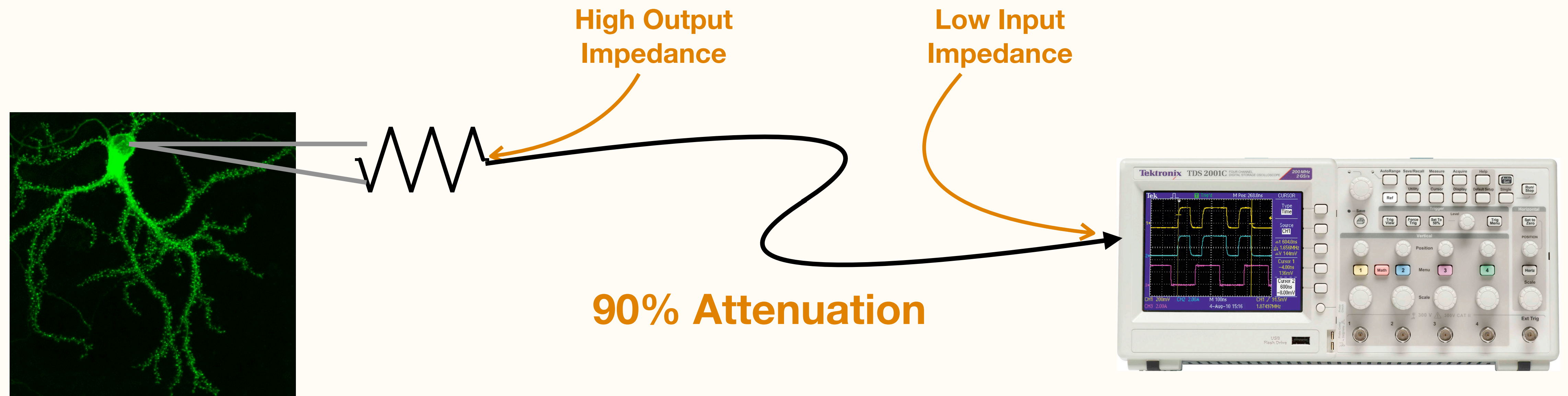


$$R_{electrode} \approx 10M\Omega$$

$$R_{in} = 1M\Omega$$

Maximizing Signal Quality

Today:

Raw Signal

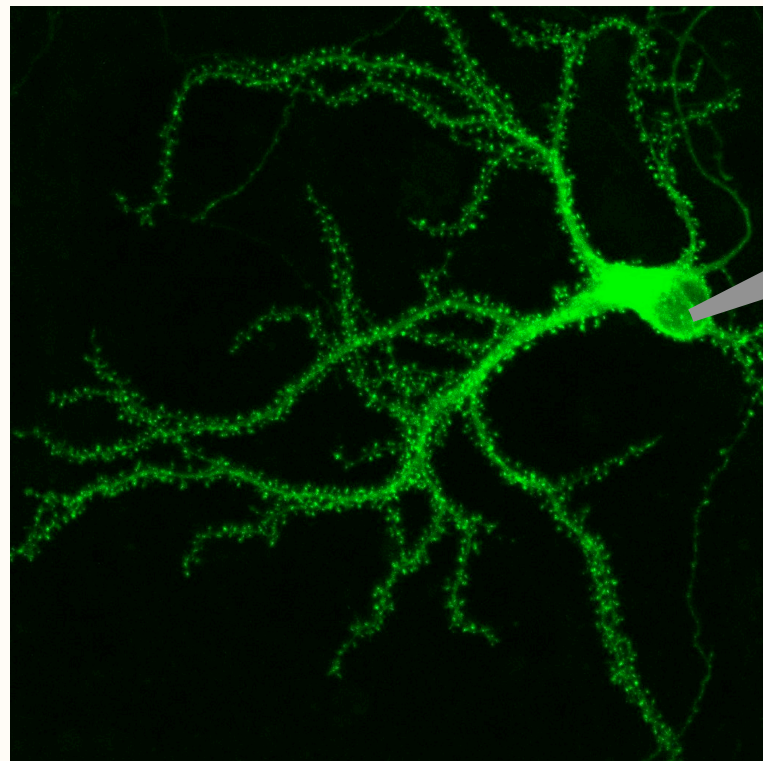

EM Pickup,
Capacitive Coupling




Poor Grounding/
Ground Loops
[Lecture 3]

Quantization Noise,
Aliasing,
Saturation/Drift
[Lecture 3]



Maximizing Signal Quality

Today:

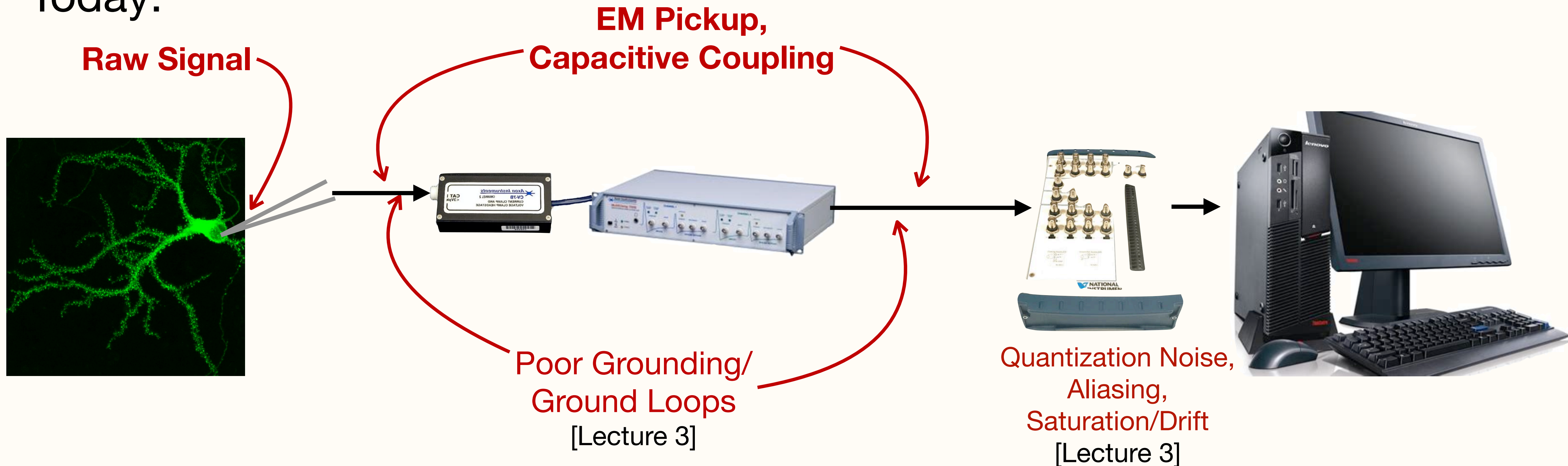

Signal to noise ratio:


$$\text{SNR} = \frac{\textit{Power}(\textit{Signal})}{\textit{Power}(\textit{Noise})} = \frac{\textit{Amplitude}(\textit{Signal})^2}{\textit{Amplitude}(\textit{Noise})^2}$$

Raw Signal Quality

It's always best to start with a clean raw signal (with large SNR) than to try to “fix” it with hardware or software


- Minimize environmental noise
 - Eliminate stray light, vibrations, electrical noise sources
- Maximize signal:
 - Healthy preparation/sample
 - Imaging: clean optics, good lighting, high contrast
 - Electrophysiology: good cell, high-quality electrode, good seal, etc

Stray Capacitance

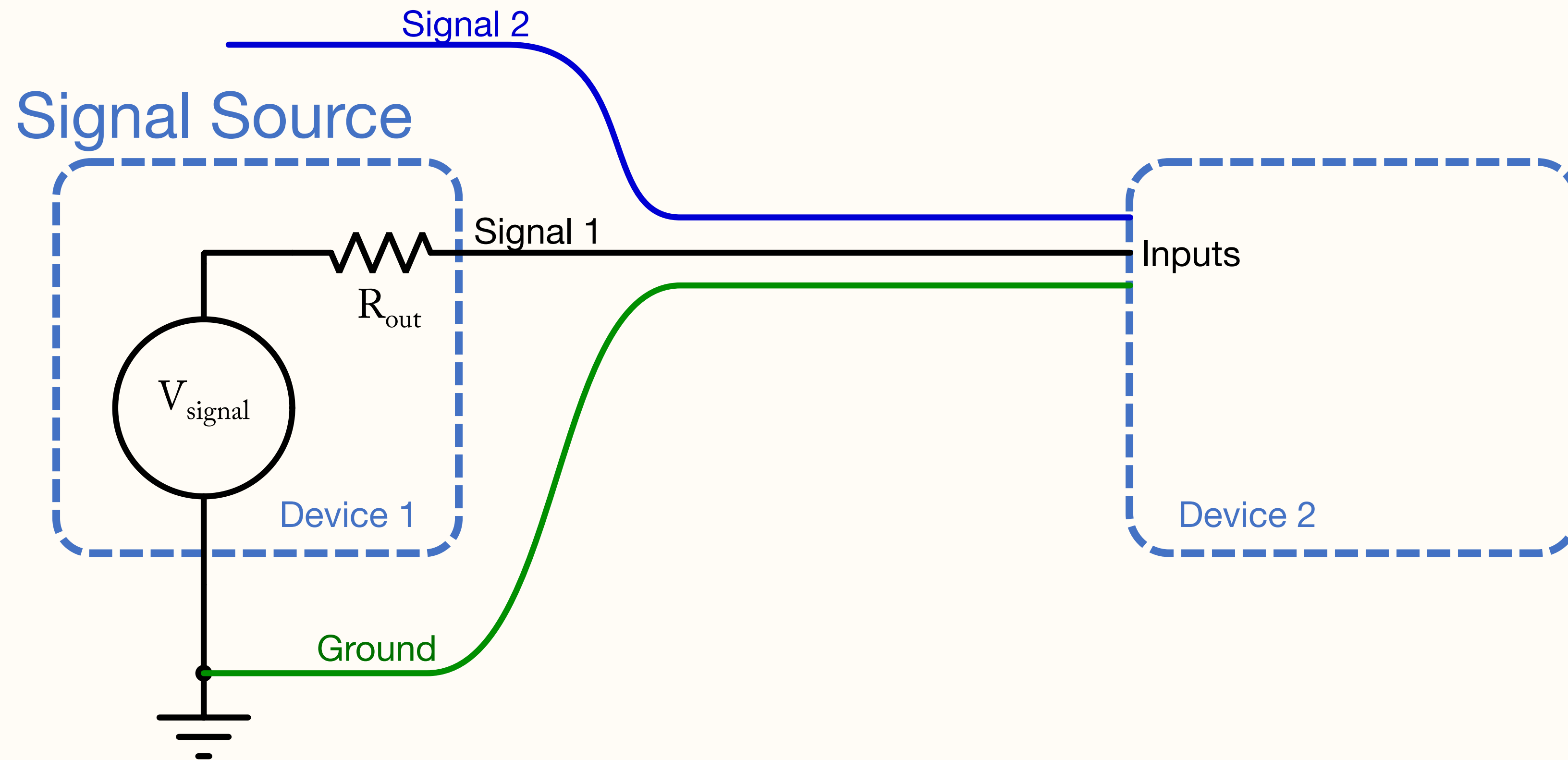


Unintended capacitance is present when two signal line run side-by-side
Or when a signal runs alongside ground

Stray Capacitance

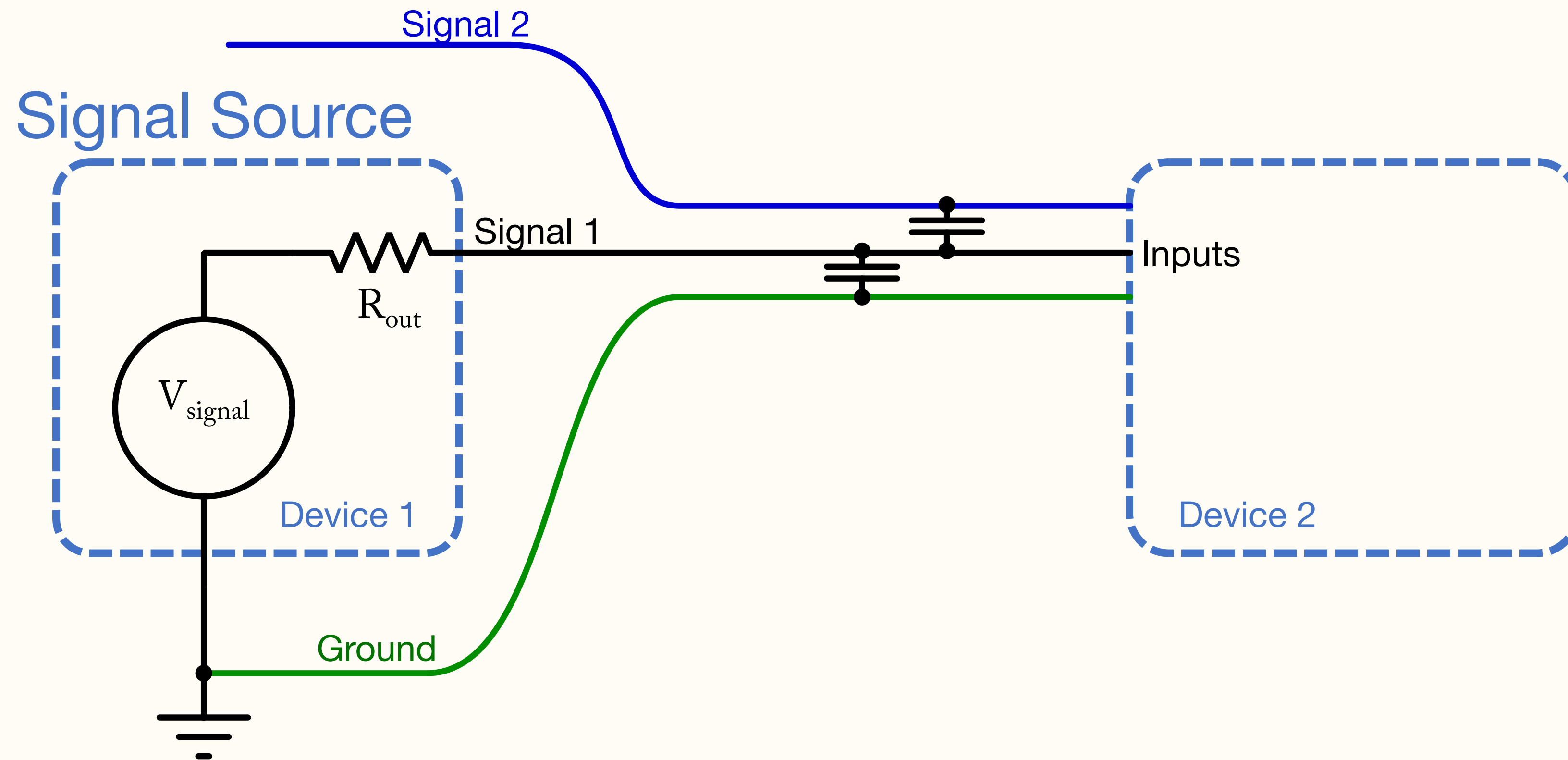


Unintended (stray) capacitance can arise: $C \propto \frac{\text{Area of overlap}}{\text{Distance between conductors}}$

Stray Capacitance

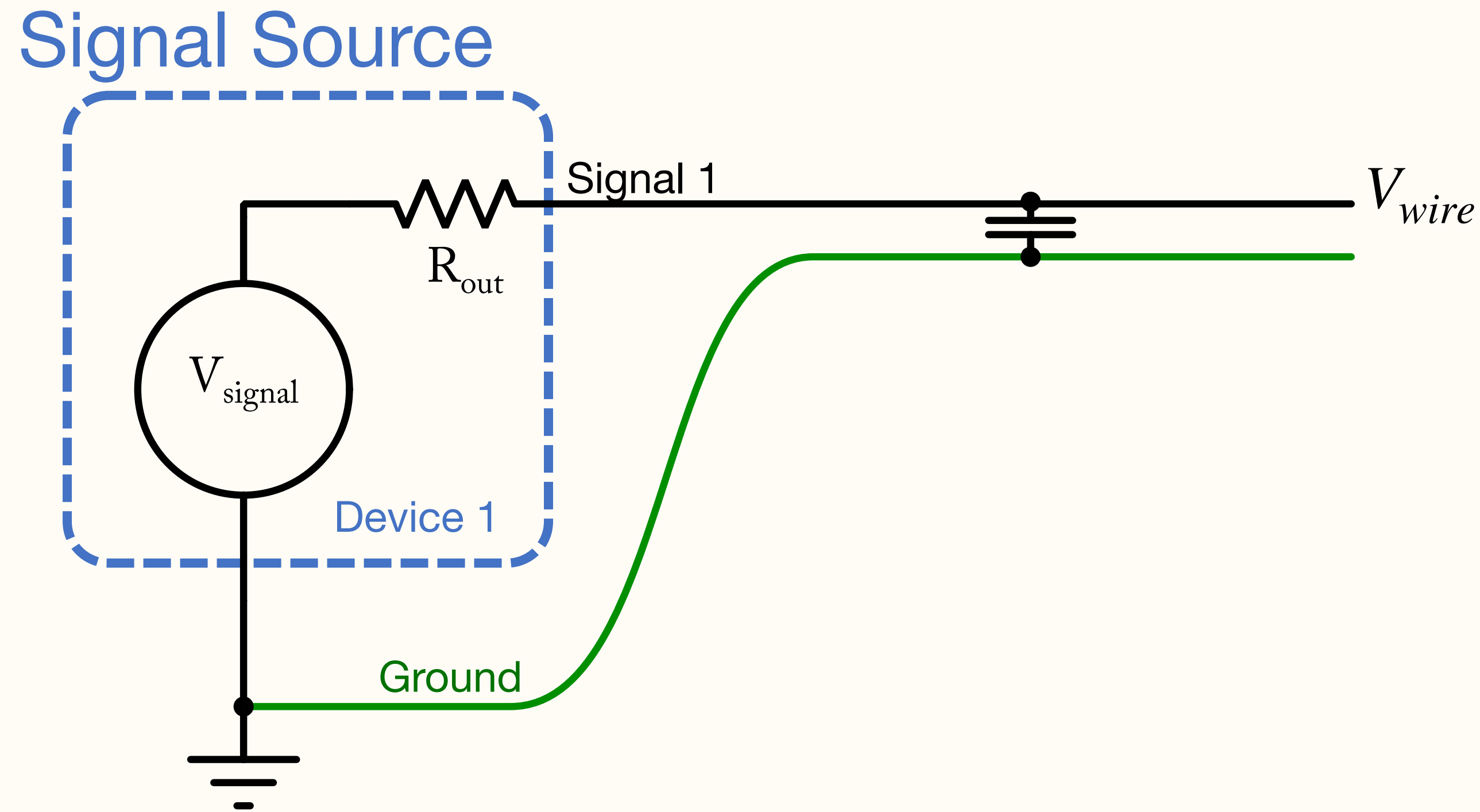


Stray capacitance to ground: Recognize the circuit motif?

Stray Capacitance

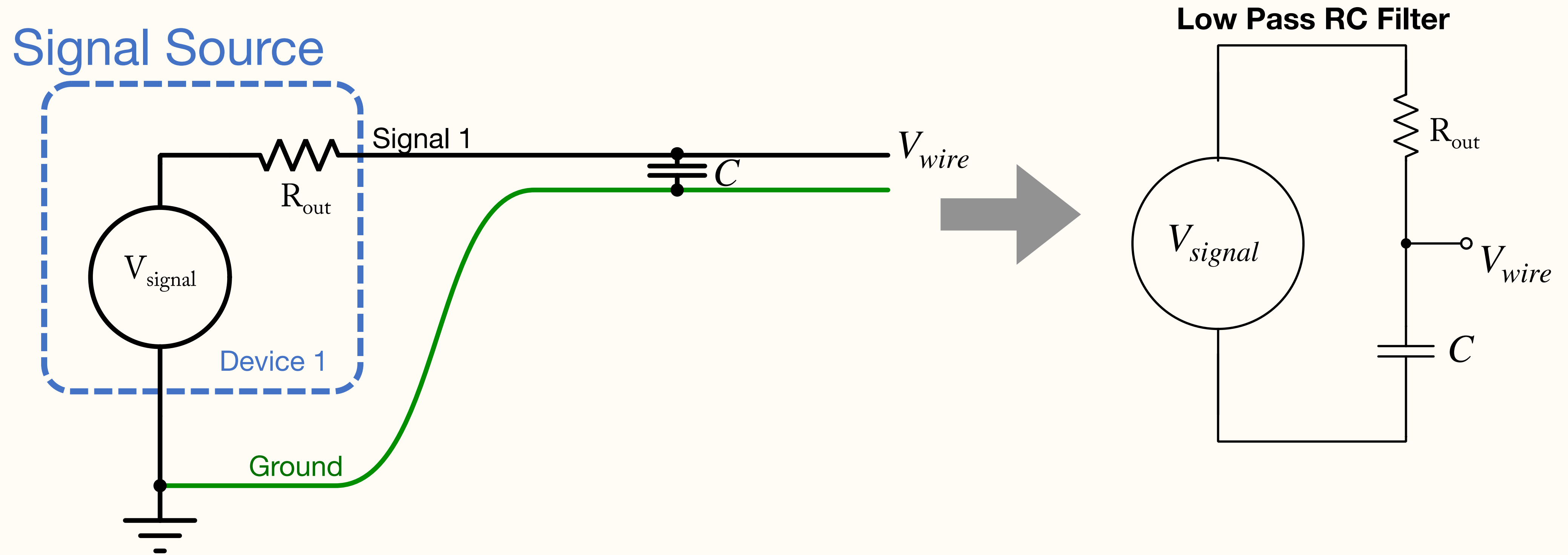

Stray capacitance to ground: **Low-pass RC filter**

Stray Capacitance

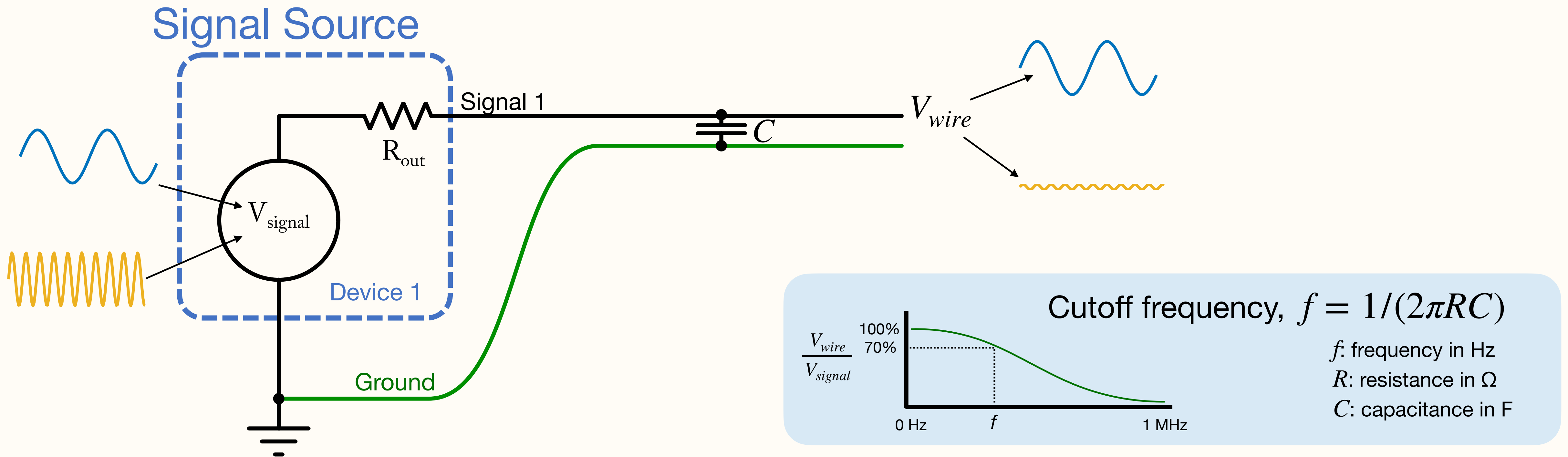

Stray capacitance to ground: **Low-pass RC filter**

- Effect is stronger for larger values of **R** and **C**


Stray Capacitance: Example & Solutions

Stray capacitance to ground: **Low-pass RC filter**

- Effect is stronger for larger values of **R** and **C**

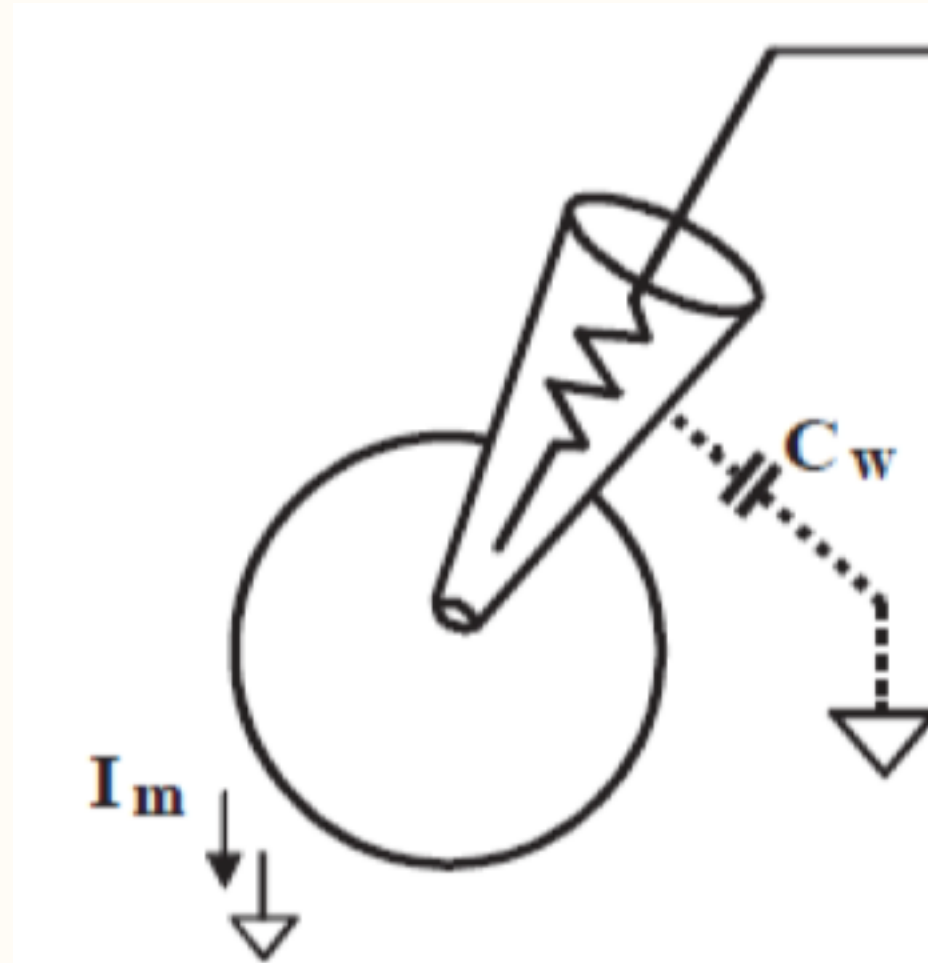Examples


- High impedance signals are particularly sensitive
- Capacitance between pipette and bath



Mitigation Strategies


- For glass electrodes
 - Reduce overlap area (lower bath level)
 - Increase distance (coat with Sylgard)
- Keep high-impedance signal lines short

Capacitive Coupling

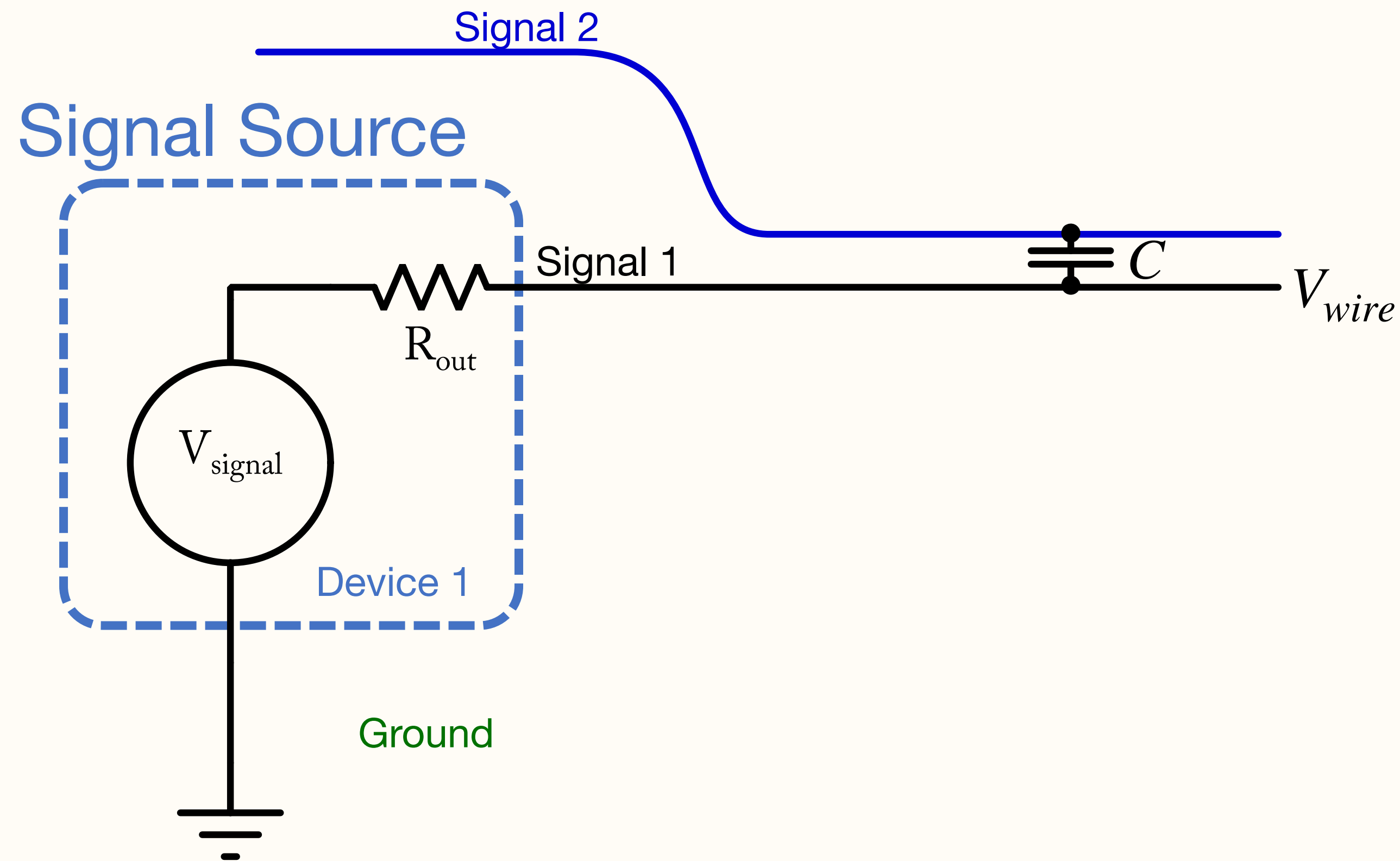

Stray capacitance between signal lines:


Capacitive Coupling

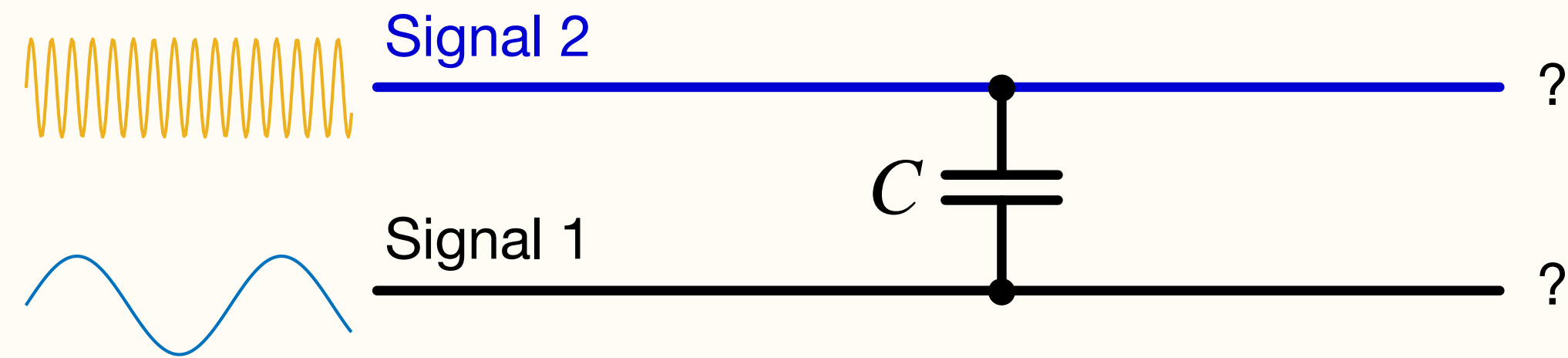

Stray capacitance between signal lines

(Capacitor acts as a selective conductor for high frequencies)


Capacitive Coupling

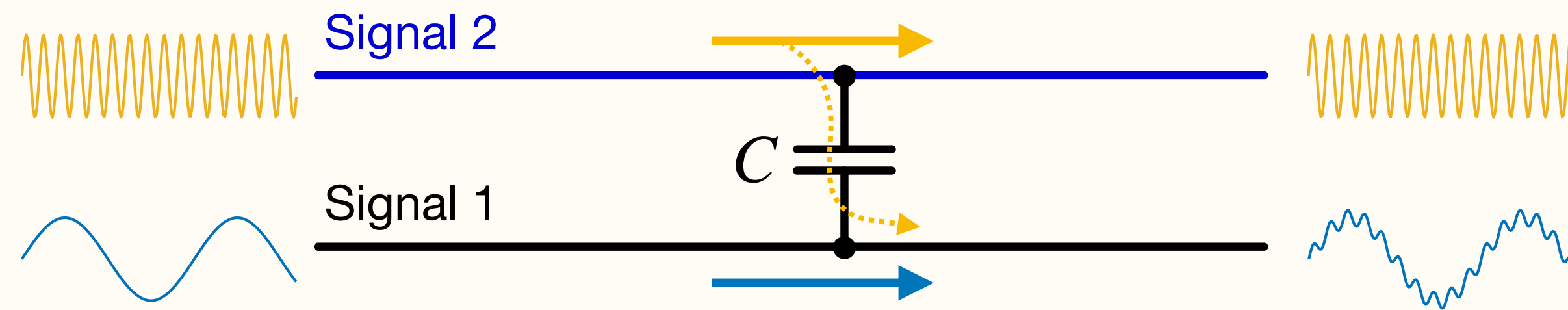

Stray capacitance between signal lines:

- Signal coupling (cross-talk) at high frequencies
(Capacitor acts as a conductor for high frequencies)


Capacitive Coupling

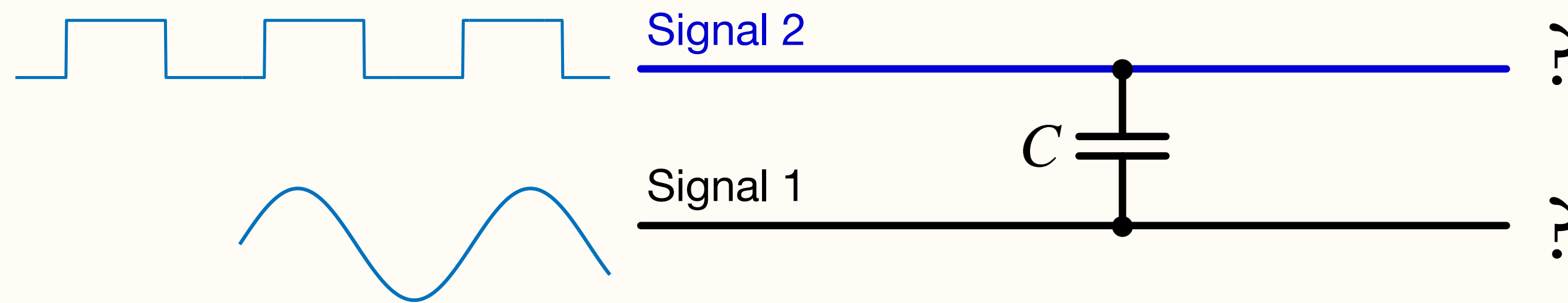


Stray capacitance between signal lines:

- Signal coupling (cross-talk) at high frequencies
(Capacitor acts as a conductor for high frequencies)

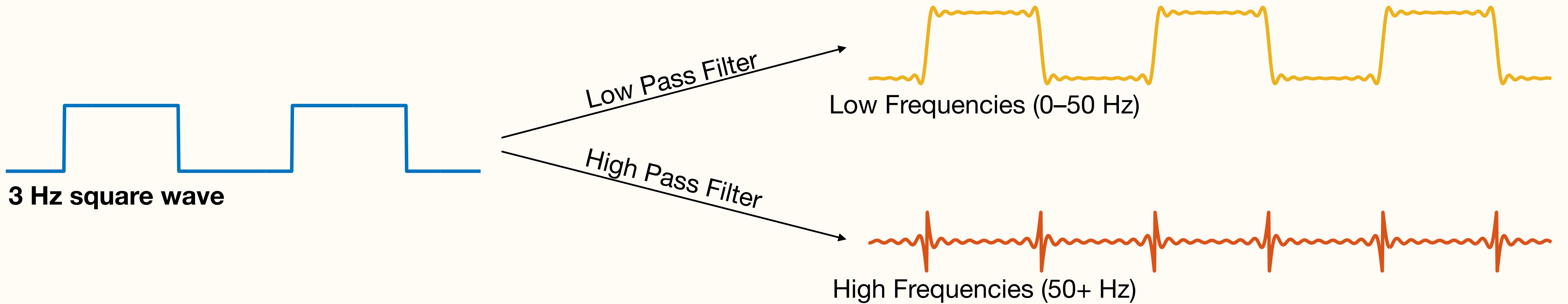
Complex Signals Are Composed of Multiple Frequencies



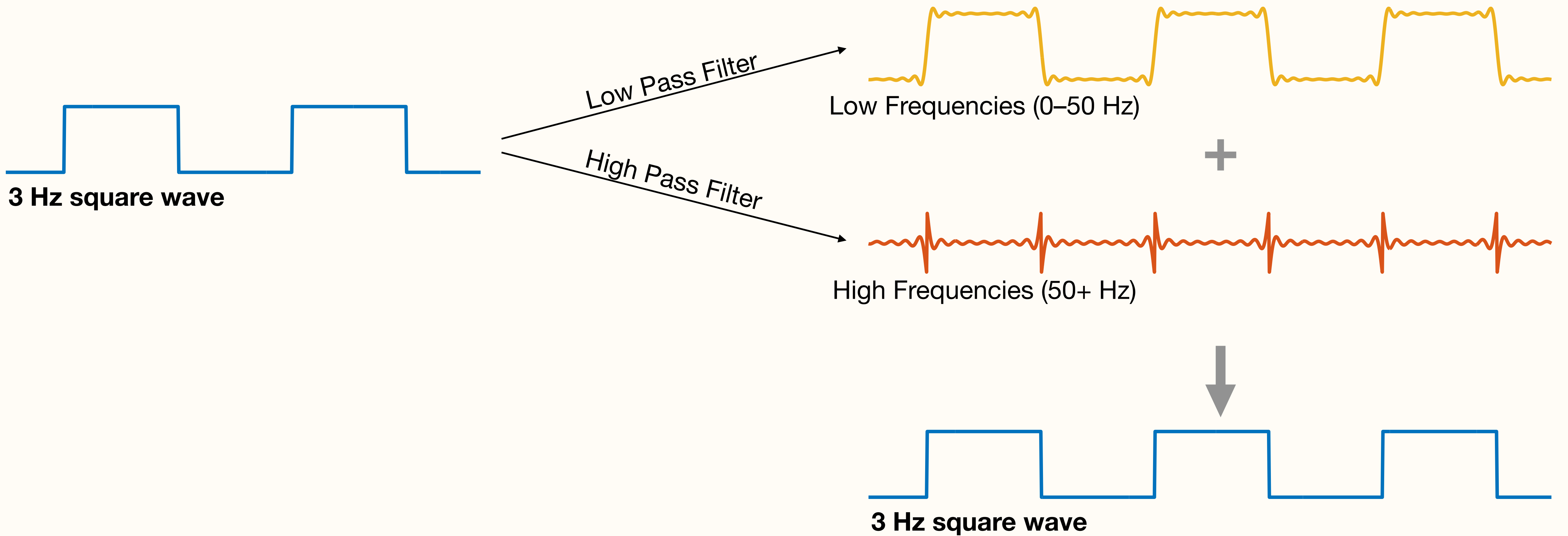Complex Signals Are Composed of Multiple Frequencies



Capacitive Coupling

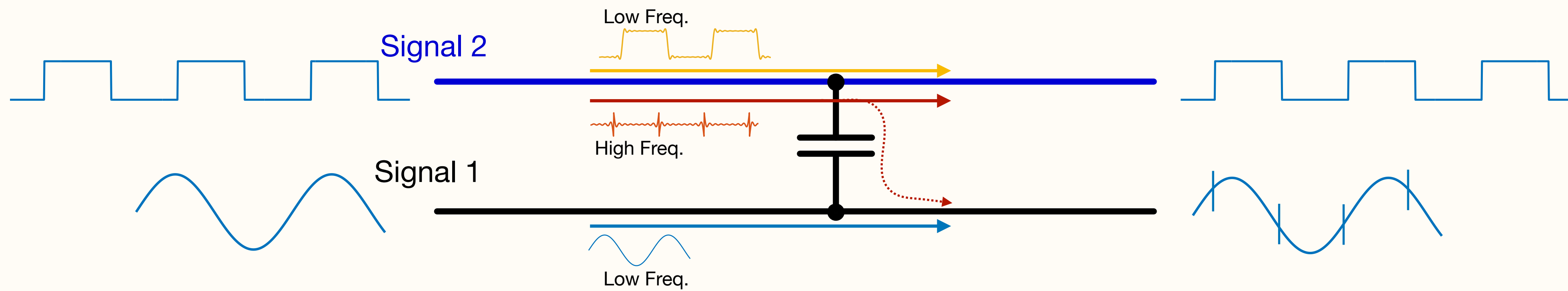

Stray capacitance between signal lines:

- Signal coupling (cross-talk) at high frequencies
(Capacitor acts as a conductor for high frequencies)

Capacitive Coupling: Example & Solutions

Examples

- High impedance signals are particularly sensitive
- Digital signals have high frequency components
(Fast transitions between 0 and 1)
- High frequency switching in some power supplies

Mitigation Strategies

- Keep sensitive analog signals away from digital lines
- If you suspect capacitive coupling:
 - Reduce path lengths
 - Increase inter-wire spacing

Antennas & EM Pickup



Electromagnetic (EM) radiation

- EM waves are emitted by time-varying currents (in nearby equipment)
- Steady (DC) voltages and current are not culprits for EM noise
- Dynamic signals (digital lines, many power supplies), especially with large currents (motors) are common sources of unwanted radiation

Wires act as antennas

- Wires pick up EM radiation and convert it into time-varying currents
- These currents will generate voltages as they flow through resistance in the circuit ($V = IR$)
- High-impedance signal sources will exhibit larger amplitude noise

Motor
(Large oscillating currents)

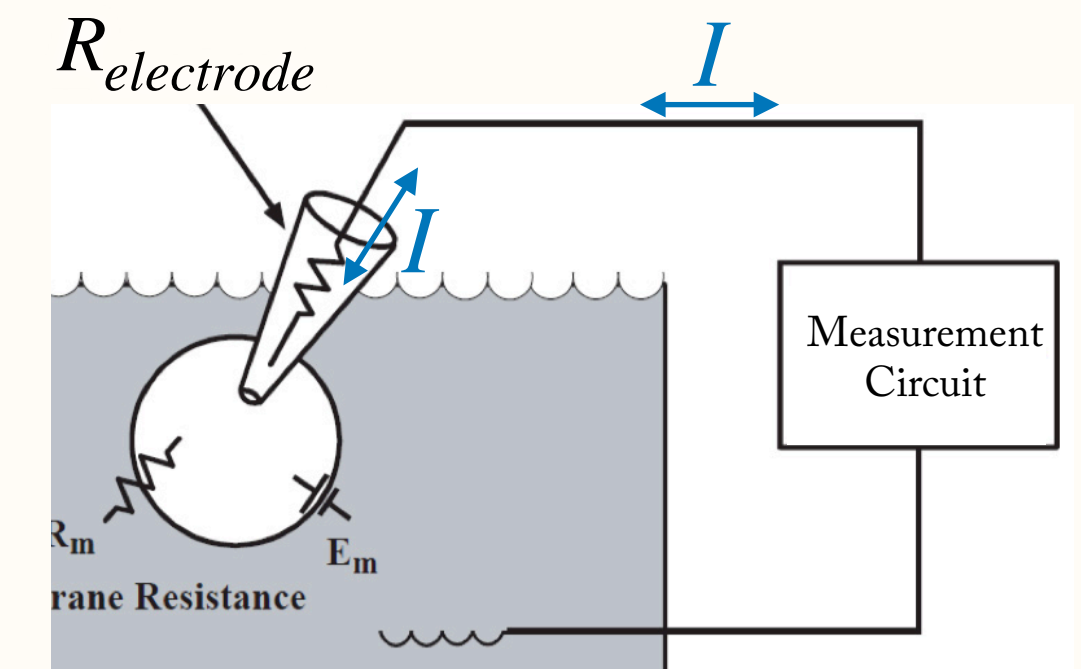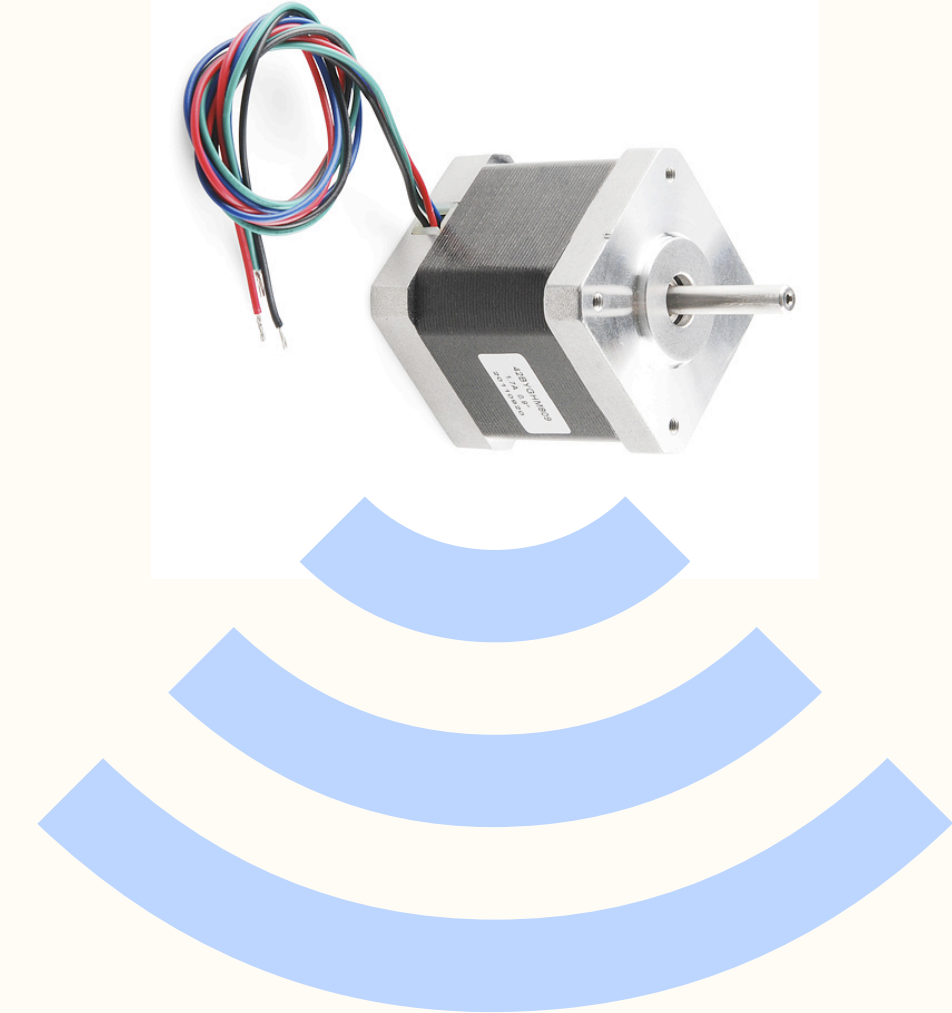

Antennas & EM Pickup

Solutions

- Separate EM radiation sources from sensitive electronics
 - E.g., power supplies, motors, AC power cables, digital circuits
 - Hint: 60 Hz noise is often a sign of EM pickup
- Shielding: Faraday cage, coaxial cables (e.g., BNC), aluminum foil
 - Avoid AC power cords inside Faraday cage
 - Avoid antennas that exit the Faraday cage (e.g. perfusion lines)
 - Grounded shields are typically better
- Pay attention to high output impedance signals
 - Minimize length of output high impedance lines
 - Keep them shielded
 - **Amplifiers** can “convert” from high to low impedance signal
- Increase signal amplitude (to increase SNR)
 - A 50 mV signal is swamped by 10 mV noise; a 5 V signal might be OK
 - **Amplifiers** can increase the voltage gain

Motor
(Large oscillating currents)

